



## Finolex Academy of Management and Technology, Ratnagiri

### Department of Information Technology

<b>Subject:</b>	<b>LOGIC DESIGN (ITC 302)</b>		
<b>Class:</b>	<b>SE IT / Semester – III (CBGS) / Academic year: 2017-18</b>		
<b>Name of Student:</b>			
<b>Roll No:</b>		<b>Date of performance (DOP) :</b>	
<b>Assignment/Experiment No:</b>	<b>8</b>	<b>Date of checking (DOC) :</b>	
<b>Title: Working with IP tables</b>			
<b>Marks:</b>		<b>Teacher's Signature:</b>	

**1.Aim:** Perform D to T FF and JK to T FF conversion.

**2. Prerequisites:**

Logic gates, FF and their conversions

**3. Hardware Requirements:**

1. IC 7473, 7374, 7486
2. Digital Trainer kit
3. Breadboard and connecting wires, probes

**4. Software Requirements: --**

**5. Learning Objectives:**

1. To understand what is FF
2. To understand how to perform D to T FF and JK to T FF conversion.

**6. Course Objectives Applicable: CO 4, CO 5**

**7. Program Outcomes Applicable:**

**8. Program Education Objectives Applicable:**

**9. Theory:** <Preferably given as handwritten work for students>

**10. Results:**

<Source code and screenshots of the output to be added here.>

**11. Learning Outcomes Achieved**

1. Understanding mounting of logic circuit on breadboard
2. Understanding of what is FF
3. Understanding of how to perform D to T FF and JK to T FF conversion.

**12. Conclusion:**

### 13. Experiment/Assignment Evaluation

SR	Parameters	Weight	Excellent	Good	Average	Poor	Not as per requirement
		Scale Factor ->	5	4	3	2	0
1	Technical Understanding	25					
2	Performance / Execution	25					
3	Question Answers	20					
4	Punctuality	20					
5	Presentation	10					
	Total out of 100 --> #(to be converted as per term-work evaluation applicable to the subject)		$\Sigma (\text{Weight} * \text{Scale Factor})/5 = \underline{\hspace{2cm}}$				

### References:

[1] Fundamentals of digital circuits by A. Anand Kumar.

### Viva Questions

1. What is mean by logic gates?
2. Explain gates with TT and Symbol.
3. What is FF?
4. How to perform D to T FF and JK to T FF conversion explain with TT.